
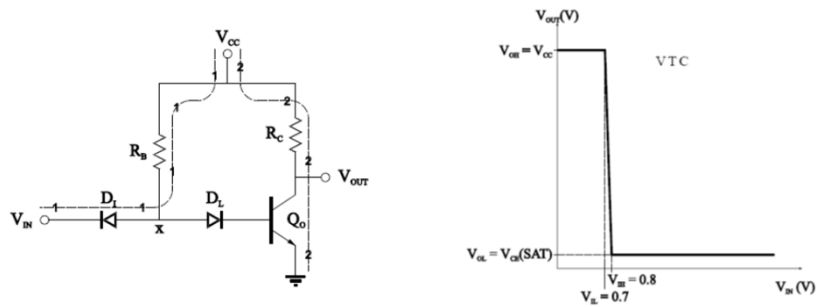


Diode-Transistor Logic (DTL)


Basic DTL Inverter

 


Basic DTL NAND Gate



Diode Modified DTL Inverter

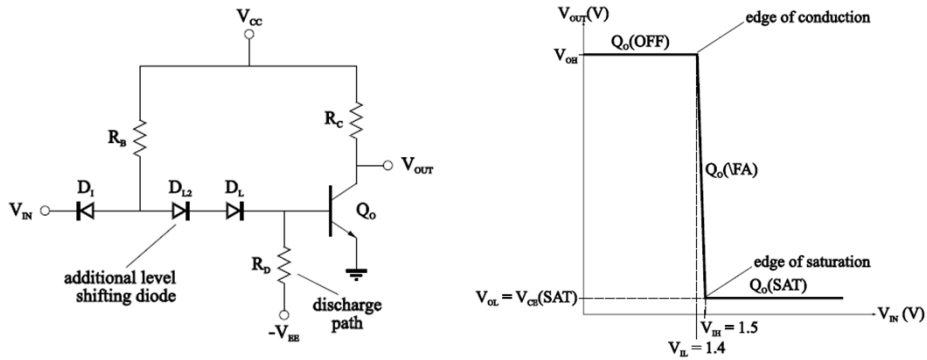


Transistor Modified DTL Inverter

 

Element	Purpose
D_1	Input diode, limits I_{IL} and provides ANDing
ρR_b	Limits I_{IL}
$(1-\rho)R_b$	Self biases Q_L
Q_L	Base-emitter level-shifting for shift of transition width and provides base driving current to Q_O
D_L	Level-shifting diode for shift of transition width
R_p	Provides discharge path for saturation stored charge removal from base of Q_O
Q_O	Output inverting BJT and output low driver for current sinking pull-down
R_c	Passive current sourcing pull-up

Element	V_{OH}	V_{OL}
D_1	On	Cutoff
Q_L	Cutoff	Forward active
D_L	Cutoff	On
Q_O	Cutoff	Saturated

VTC of Transistor Modified DTL Inverter

 

$$V_{OH} = V_{CC}$$


$$V_{IL} = V_{BE,O(FA)} + V_{BE,L(FA)}$$

$$V_{OL} = V_{CE,O(SAT)}$$


$$V_{IH} = V_{BE,O(SAT)} + V_{BE,L(FA)}$$

DTL Fan-out

 Determined by the output low state as D_1 is off for high-inputs



Cascaded DTL

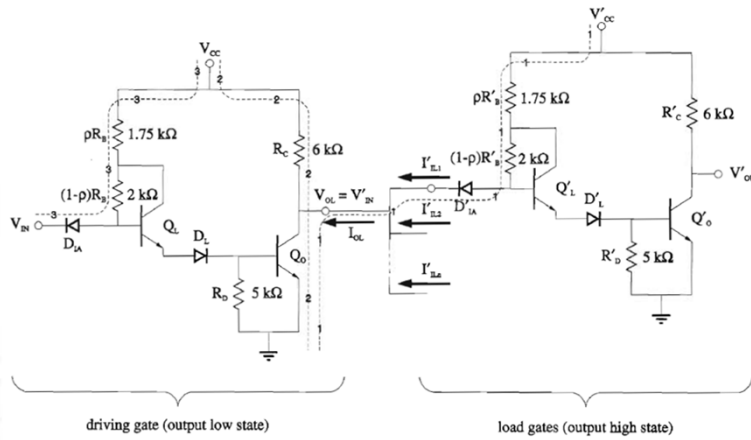

$$I_{OL} = I_{C,O(SAT)} - I_{RC}$$

$$N = \left\lfloor \frac{I_{OL}}{I_{IL}} \right\rfloor$$

$$I_{RC} = \frac{V_{CC} - V_{CE,O(SAT)}}{R_C}$$

Path 2

$$I_{C,O(SAT)} = \sigma \beta_F I_{B,O(SAT)}$$

If not given (for maximum fan-out): $\sigma = 1$

$$I_{B,O} = I_{E,L} - I_{RD}$$

$$I_{RD} = \frac{V_{BE,O(SAT)}}{R_D}$$

$$I_{E,L} \cong \frac{V_{CC} - V_{BE,L(FA)} - V_{D,L(ON)} - V_{BE,O(SAT)}}{\rho R_B}$$

$$I_{IL} = \frac{V_{CC} - V_{D,I(ON)} - V_{CE,O(SAT)}}{R_B}$$

Path 3



Example: Calculate the DTL fan-out for $\beta_F = 49$ and $\sigma = 0.85$.

Power Dissipation


Example: Calculate the average power dissipation for the above example?

Tansistor-Transistor Logic (TTL)


Basic TTL Inverter

  


Basic DTL Inverter (compare)

 

Basic TTL NAND Gate


 


 Actual TTL NAND Gate with Totem Pole Output



Element	Purpose
Q ₁	Multi-emitter input BJT, base-collector level shifting of transition width, pull-down of Q ₃
R _B	Limits I _{IL}
Q ₃	Drive splitter, provides base driving current to Q _O , base-emitter level shifting for shift of transition width, pull-down of Q _P
R _C	Along with Q ₃ provides logic inversion to output-high driver
Q _O	Output inverting BJT, output low driver for current sourcing pull-down
D _L	Diode level shifting between V _{CC} and output
R _D	Provides discharge path for saturation stored charge of Q _O
Q _P	Provides active current-sourcing pull-up
R _{CP}	Part of active pull-up and limits current spikes during output high-to-low transitions
D _{C1} , D _{C2}	Input clamping diodes to limit the negative swing of the inputs to one diode drop below ground

VTC of an actual TTL Inverter

  

$$V_{OH} = V_{CC} - V_{BE,P(FA)} - V_{D,L(ON)}$$

$$V_{OL} = V_{CE,O(SAT)}$$

$$V_{OB} = V_{CC} - I_{RC}R_C - V_{BE,P(FA)} - V_{D,L(ON)}$$


$$I_{RC} = I_{RD} = \frac{V_{BE,O(FA)}}{R_D}$$

$$V_{IL} = V_{BE,S(FA)} - V_{CE,I(SAT)}$$

$$V_{IH} = V_{BE,O(SAT)} + V_{BE,S(SAT)} - V_{CE,I(SAT)}$$

$$V_{IB} = V_{BE,O(FA)} + V_{BE,S(FA)} - V_{CE,I(SAT)}$$


States of diodes and BJTs

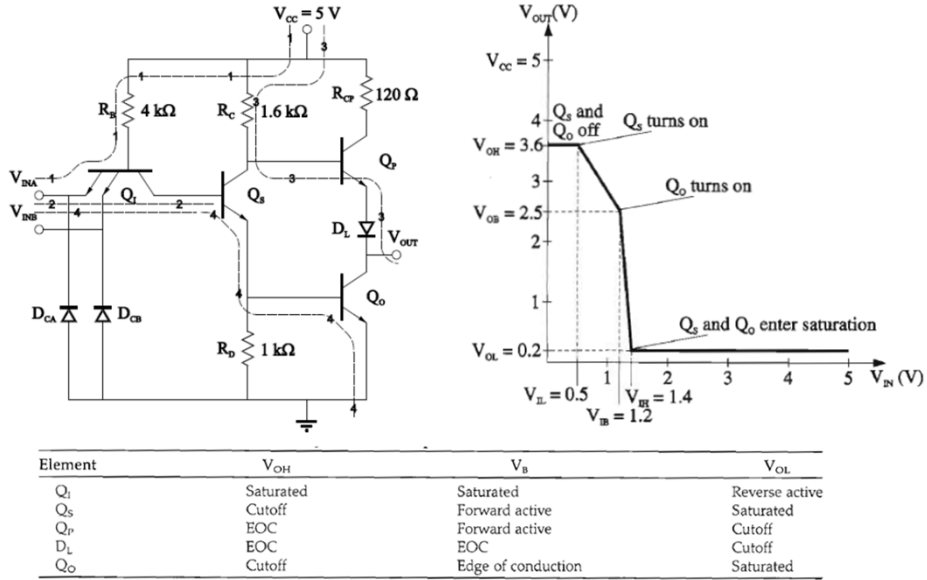


EOC: Edge of conduction

TTL Fan-out

 Determined by the output low state as Q_1 is cut-off for high-inputs



Cascaded TTL

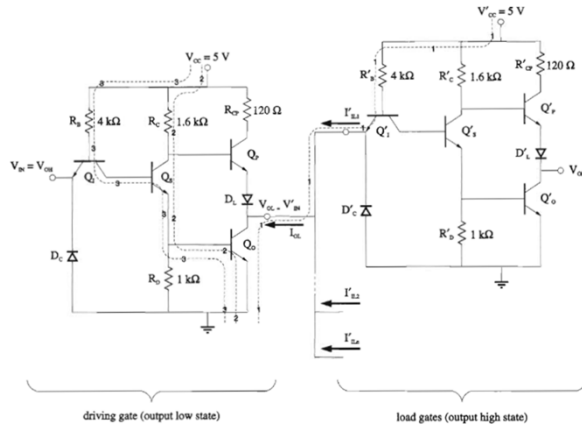

Path 1

$$I_{IL} = \frac{V_{CC} - V_{BE,I(SAT)} - V_{CE,O(SAT)}}{R_B}$$

Path 2 & 3

$$I_{E,S(SAT)} = I_{B,S} + I_{C,S}$$

$$N = \left\lfloor \frac{I_{OL}}{I_{IL}} \right\rfloor$$

$$I_{OL} = I_{C,O(SAT)} = \sigma \beta_F I_{B,O(SAT)}$$

$$I_{B,O(SAT)} = I_{E,S(SAT)} - I_{RD}$$

$$I_{RD} = \frac{V_{BE,O(SAT)}}{R_D}$$

Unless given $\sigma = 1$

$$I_{C,S} = \frac{V_{CC} - V_{CE,S(SAT)} - V_{BE,O(SAT)}}{R_C}$$

$$I_{B,S} = I_{C,I(RA)} = (1 + \beta_R) I_{B,I}$$

$$I_{B,I} = \frac{V_{CC} - V_{BC,I(RA)} - V_{BE,S(SAT)} - V_{BE,O(SAT)}}{R_B}$$

Example (TTL Fan-out)

Example: Calculate the TTL fan-out for $\beta_F = 25$, $\sigma = 0.85$ and $\beta_R = 0.1$

$$I_{RB(OL)} = 675 \mu A \quad I_{IL} = I_{RB(OH)} = 1 \text{ mA}$$

$$I_{RC(OL)} = 2.5 \text{ mA} \quad I_{OL} = 51.9 \text{ mA}$$


$$N = \left\lfloor \frac{I_{OL}}{I_{IL}} \right\rfloor = 51$$

Example (Power Dissipation)

Example: Calculate the average power dissipation for the above example?

$$P_{CC(avg)} = 10.4 \text{ mW}$$


Open-Collector TTL

 

Mostly used in data busses where multiple gate outputs must be ANDed.

- This can be accomplished by using a single pull-up resistor with open-collector TTL gates
- This type of connection is referred to as *wired-AND*.

Low Power TTL (LTTL)

 

Accomplished simply by increasing the resistance values. However this results in

- Decreased fan-out
- Longer transient-response times

Speed & Power Relationship

Family	Power	Prop. Delay
TTL	10 mW	9 ns
STTL	20 mW	3 ns
LSTTL	2 mW	9 ns
ASTTL	10 mW	2 ns
ALSTTL	1 mW	4 ns
FAST	4 mW	2 ns